


CONSIDERATIONS FOR CONSTRUCTION OF LNA / RELAY COMBINATIONS FOR EME

PRESENTED

BY MIKE MELUM, KL6M

EME-2010 DALLAS, TX

THANKS FOR HAVING US

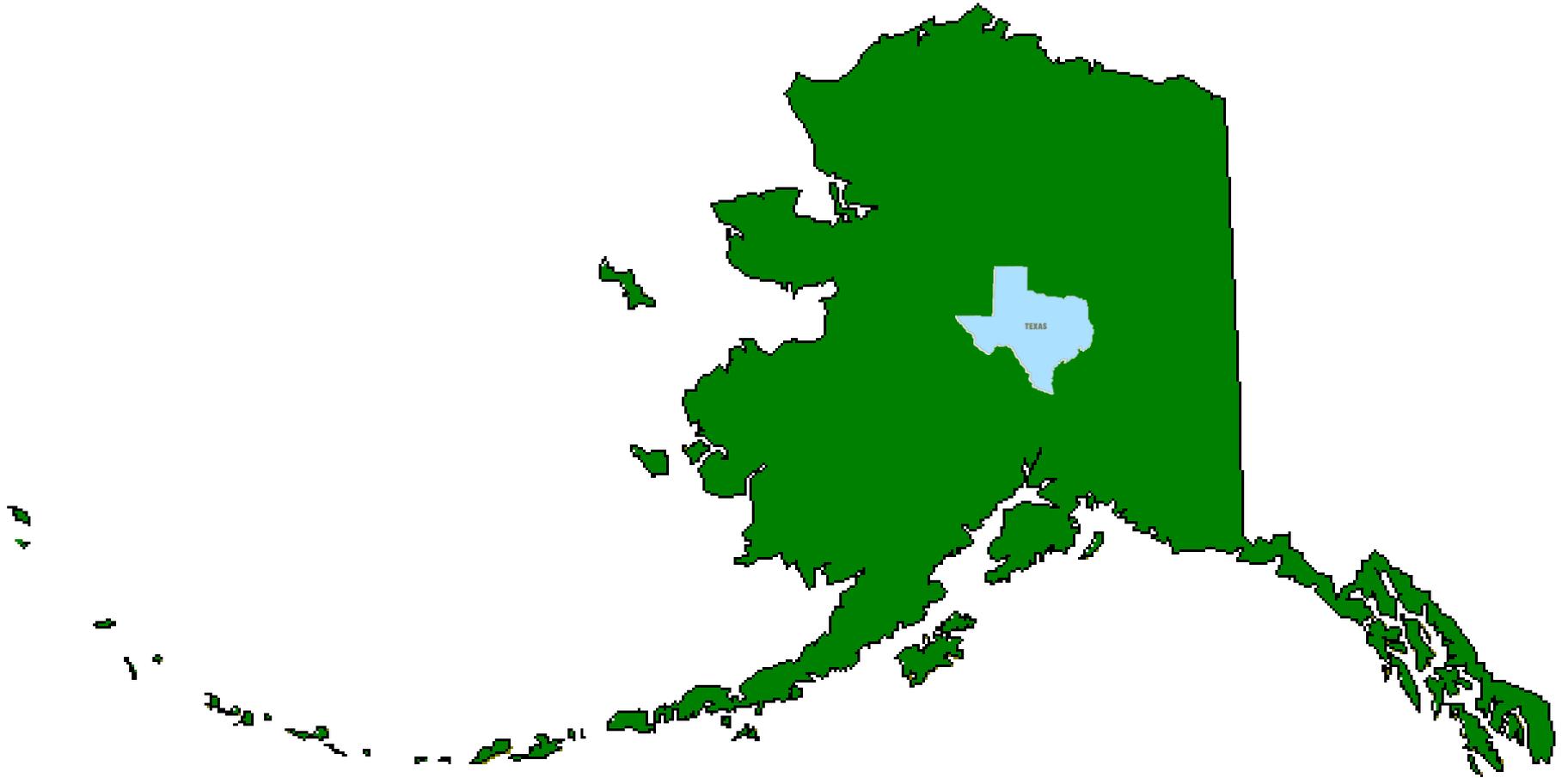


CONTENTS

- CONFIGURATIONS
- RELAY TYPES
- ENCLOSURES
- NOISE FIGURE
- CONNECTORS
- CONCLUSION

CONFIGURATIONS (#1)


#1

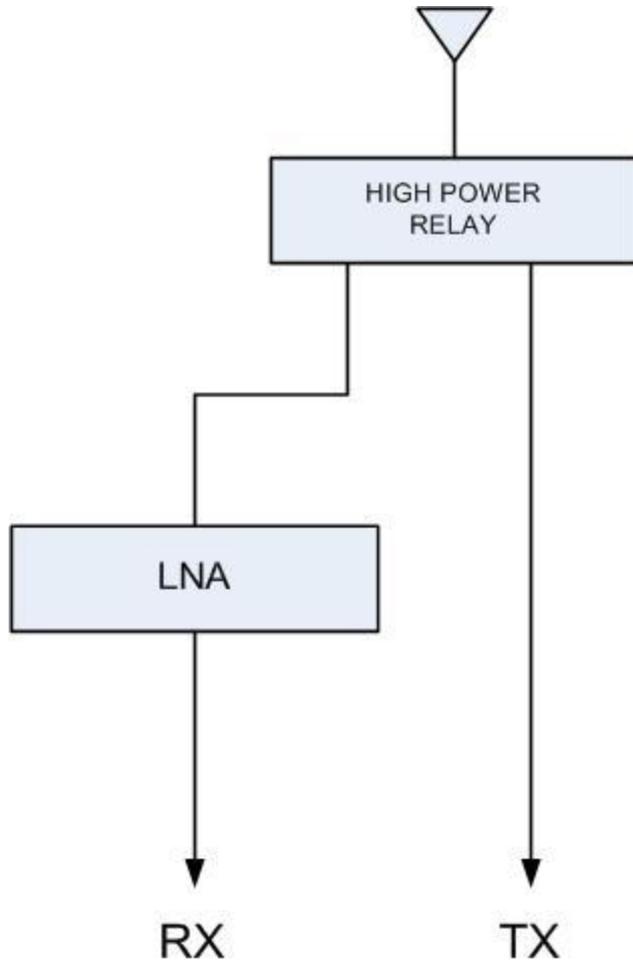

- RELAY SPECS ARE CRITICAL IN THIS CONFIG
 - POWER HANDLING
 - PRIMARILY ISOLATION
 - ASSUME MAX LNA = 0dBm
 - ASSUME 1KW (60dBm)
- DRAWBACKS
 - TWO FEEDLINES
 - NO TERMINATION FOR LNA


CONFIGURATIONS (#2)

#2

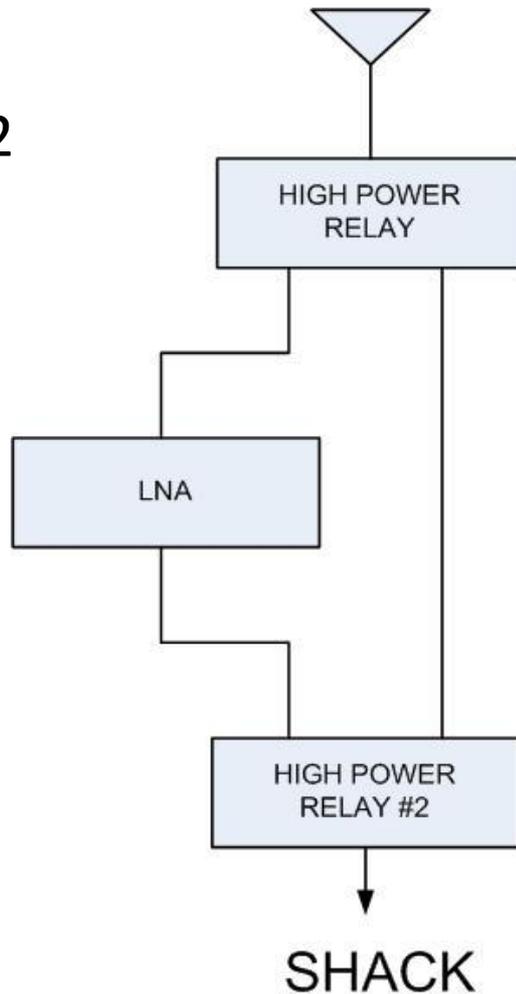

- SAME ISSUES AS #1
- ADDS ADDITIONAL RELAY
- DELETES ONE FEEDLINE
- RELAY #2 ISOLATION PROTECTS OUTPUT OF LNA
- REQUIRES ANOTHER RELAY IN THE SHACK


CONFIGURATIONS (#3)

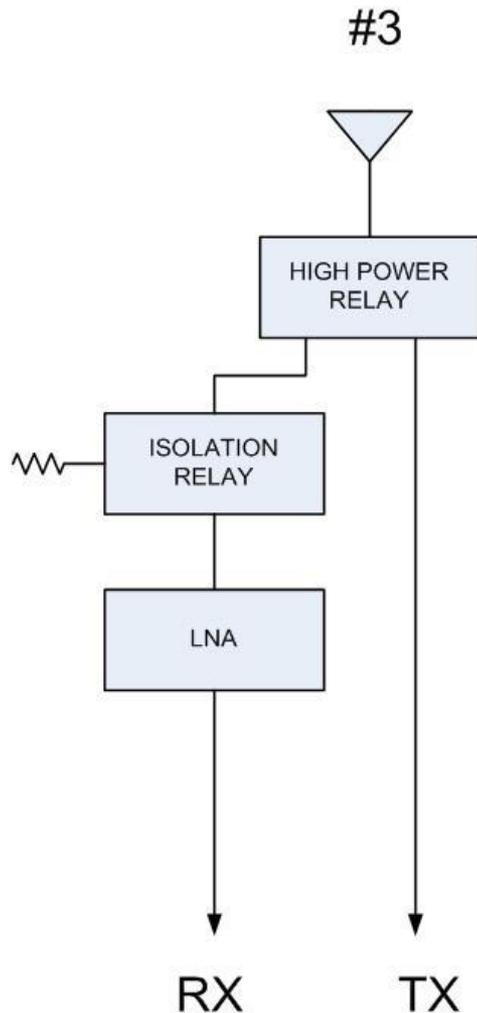

- This config is failsafe
- Provides LNA input termination
- Drawbacks
 - Two feedlines
 - Additional loss ahead of LNA
- Trade-off = safety vs performance

CONFIGURATIONS (#4)


#4

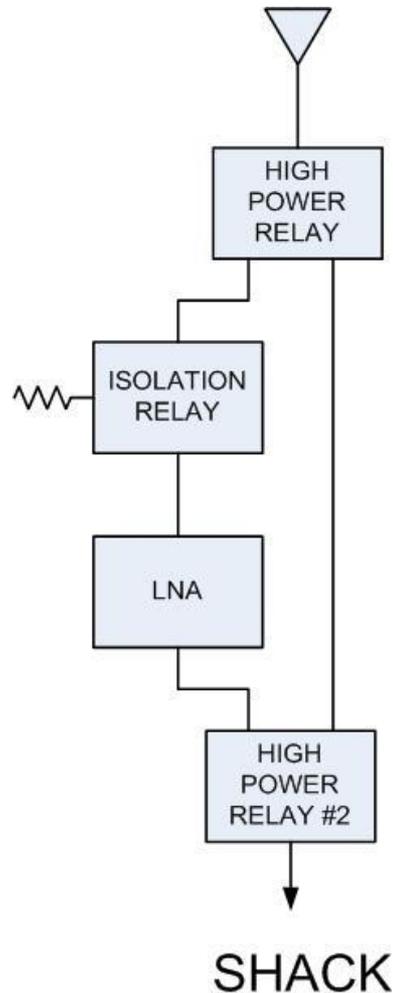

- Variation of #3
- Adds additional high power relay at the antenna
- This relay needs to have high isolation
- Drawback is the need for additional relay in the shack

CONFIGURATIONS (#5)


#5

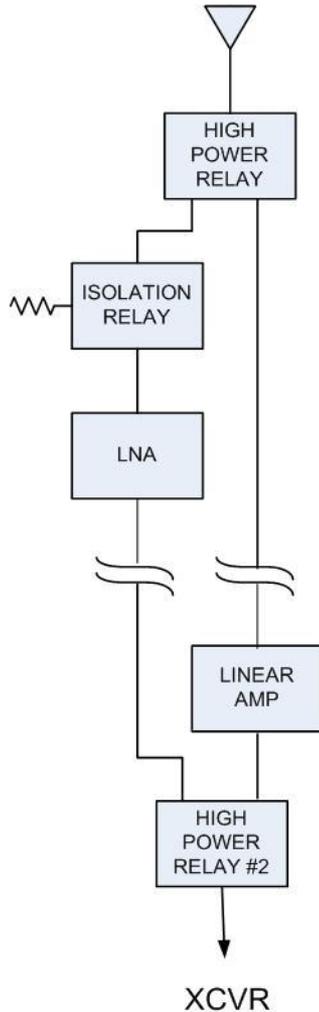

- YET ANOTHER VARIATION
- Same basic features as #3
- Two feedlines
- Relay #2 needs less isolation

RELAYS

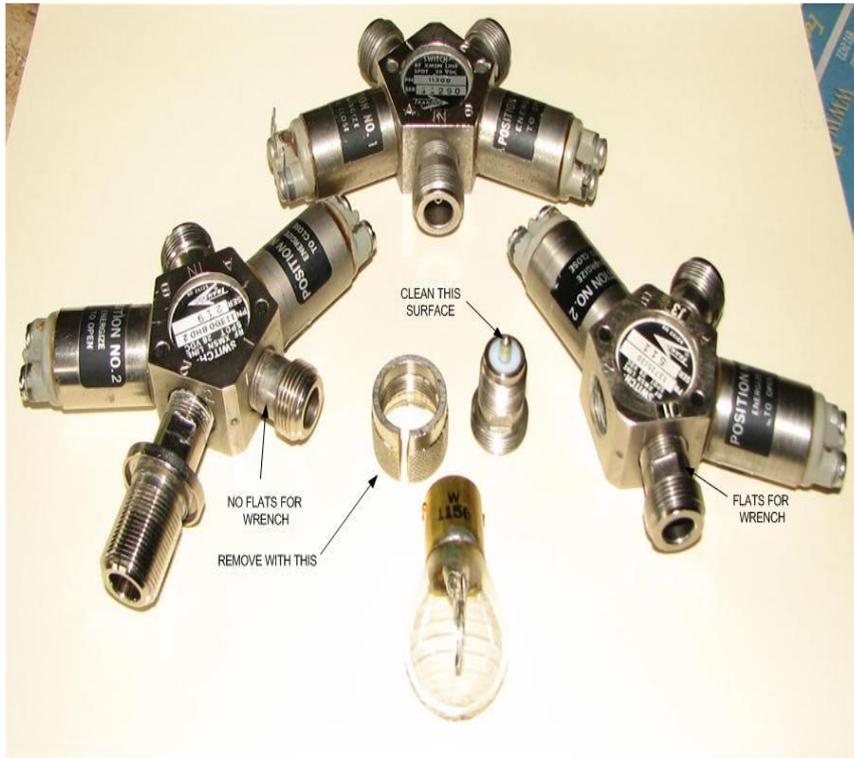- Transco-Y
 - Designed in 1950's
 - Available
 - Low loss (0.05dB)
 - High Isolation (60dB)
 - High Power Capability (>KW)




RELAYS


- More about the Transco-Y
 - Check ‘em...they are old!
 - DC resistance of contacts < 0.2 Ohms
 - Intermittent or > 0.2 Ohms = Service!
 - Remove connectors and clean contacts
 - Solvent and steel wool
 - N-C coils - Energize coil to reassemble
 - Coil replacement may require heating of set screws

RELAYS



- Electric Burnishing of Contacts

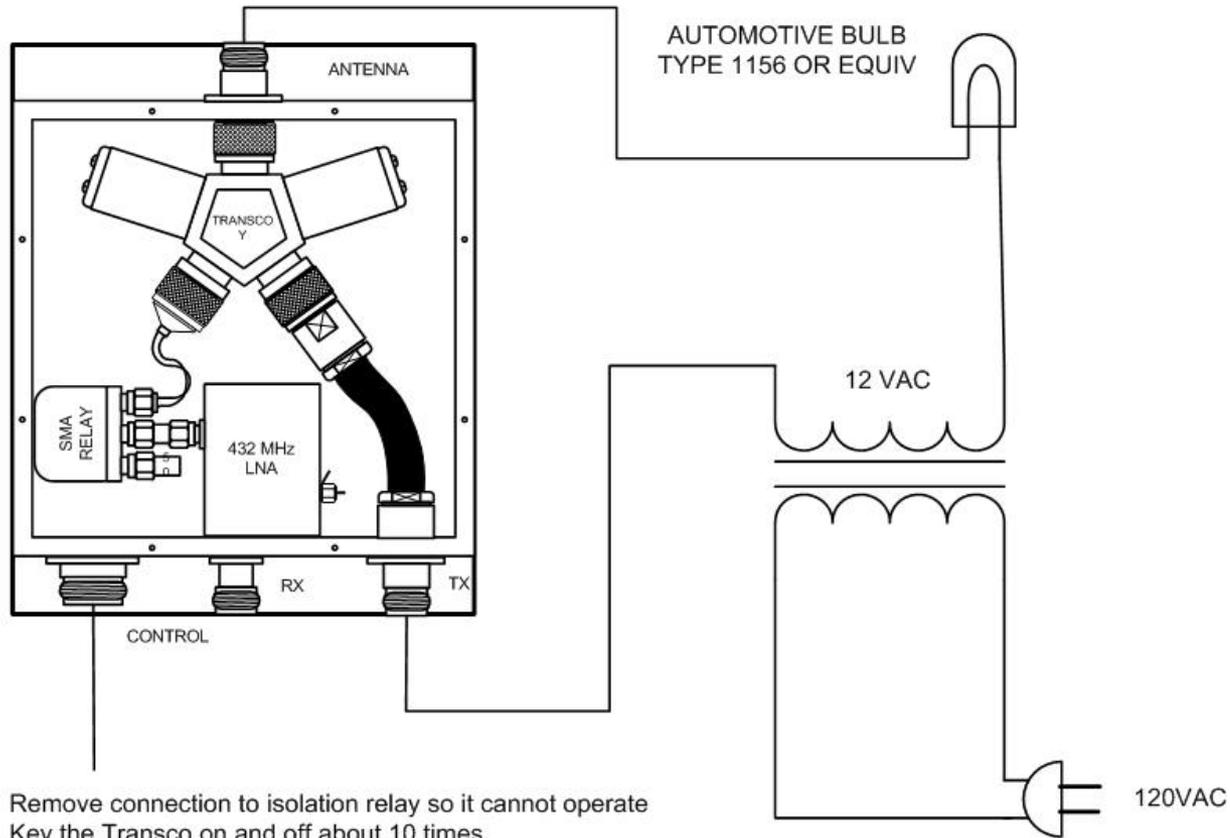

More Relays

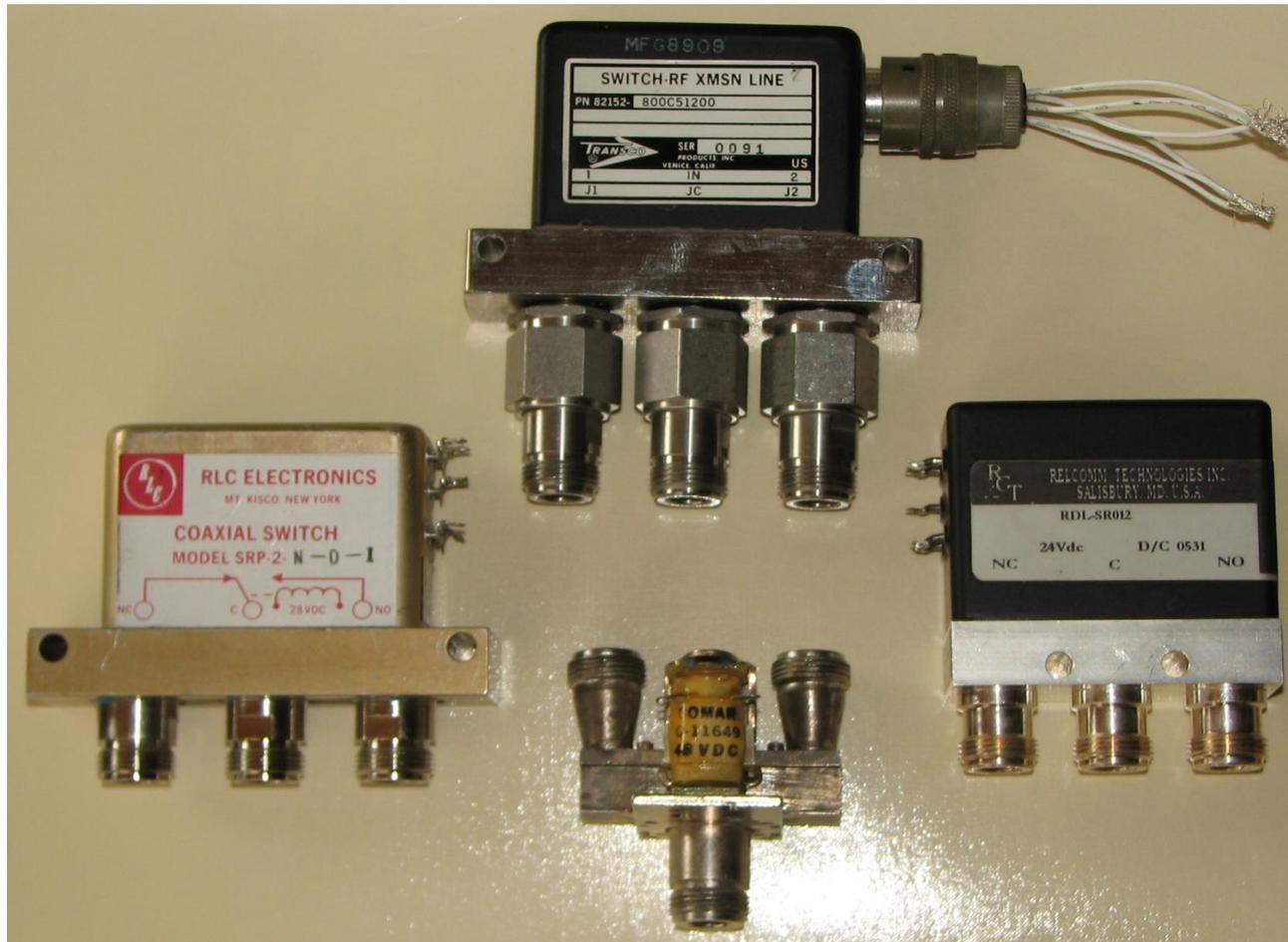

ENCLOSURES

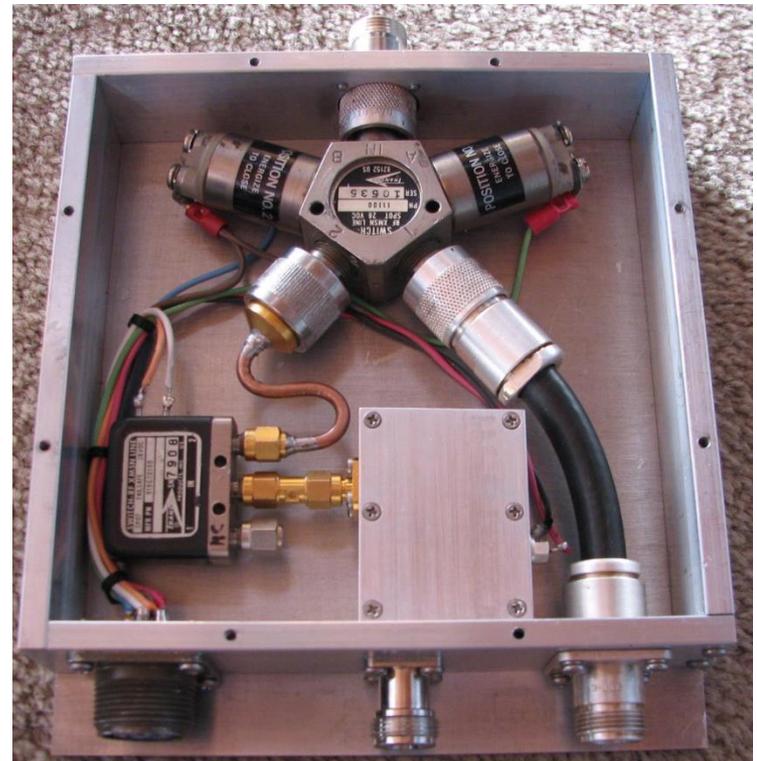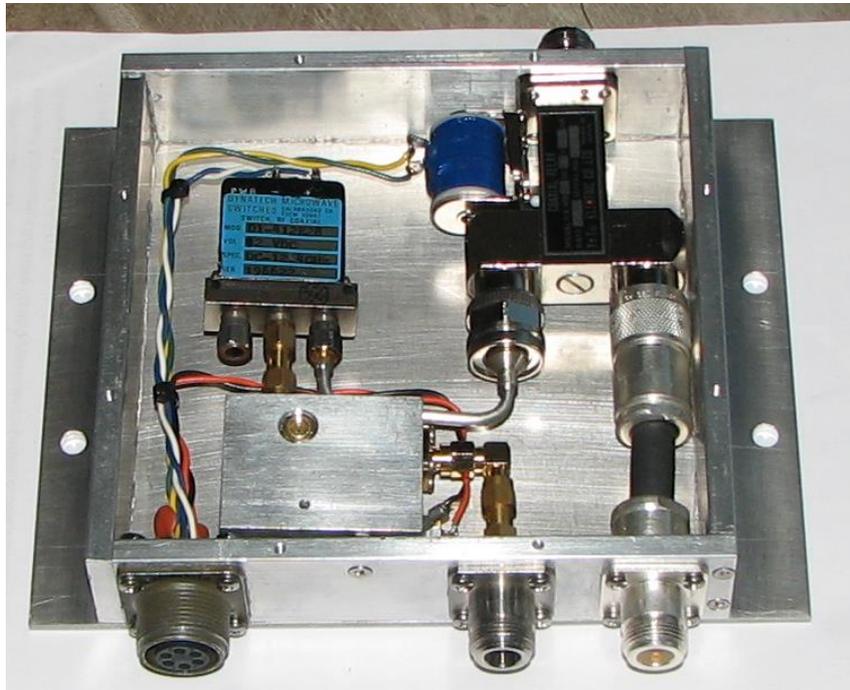


ENCLOSURES

- FOCUS
 - ACHIEVE LOWEST LOSS AHEAD OF LNA AS POSSIBLE (ALTHOUGH I CHOOSE TO USE AN ISOLATION RELAY)
 - MINIMIZE SIZE AND WEIGHT
 - MAXIMIZE WEATHER RESISTANCE
 - Weep holes?
 - Silicone sealer

ENCLOSURES


- MY 432 MHz System

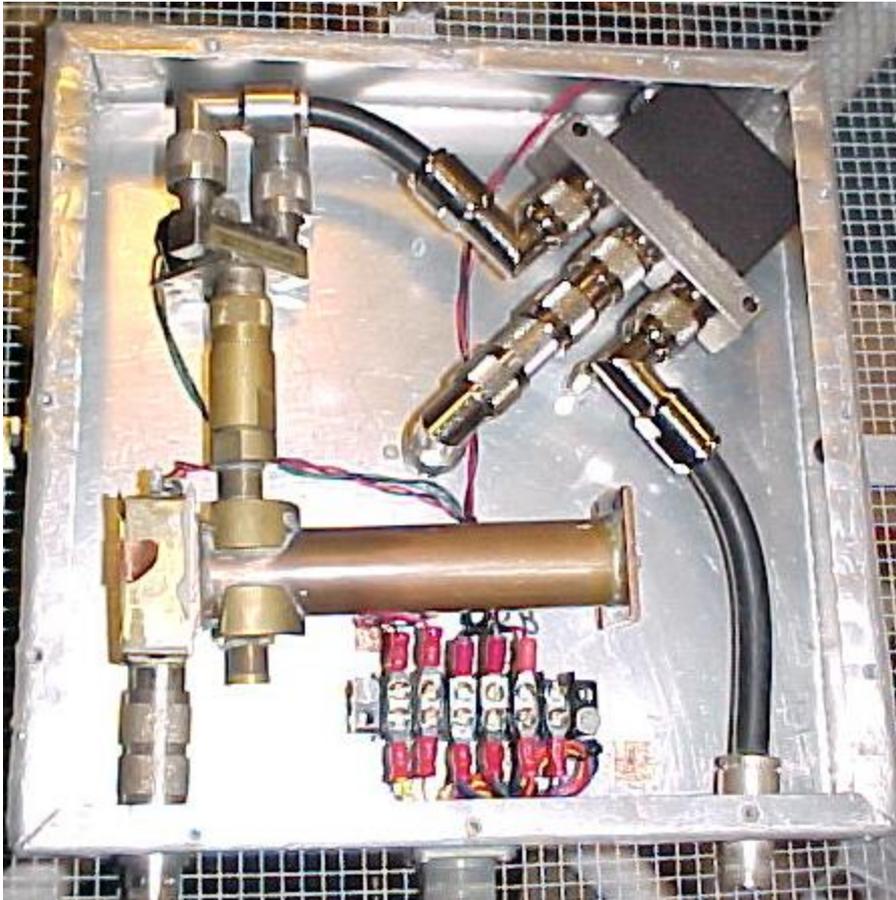

LNA NOISE FIGURE = 0.17dB

OVERALL NOISE FIGURE = 0.37dB

NOISE FIGURE (OF MY SYSTEM)

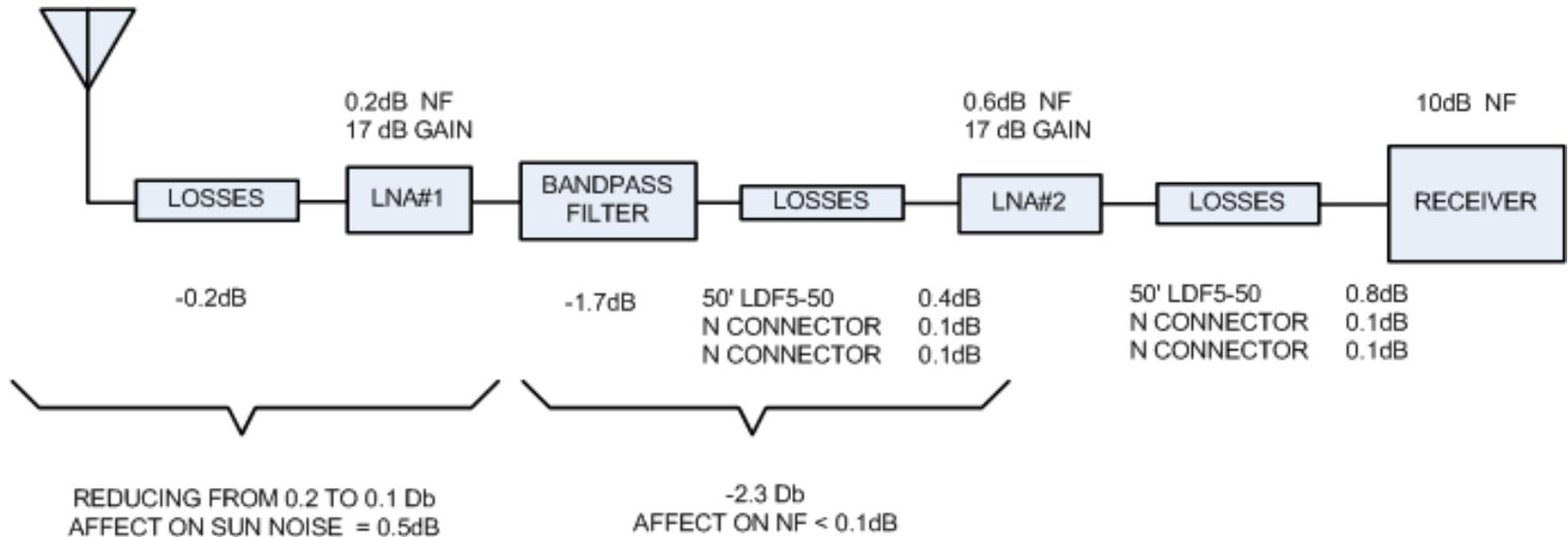



CONNECTORS




#3

CONNECTORS


#5

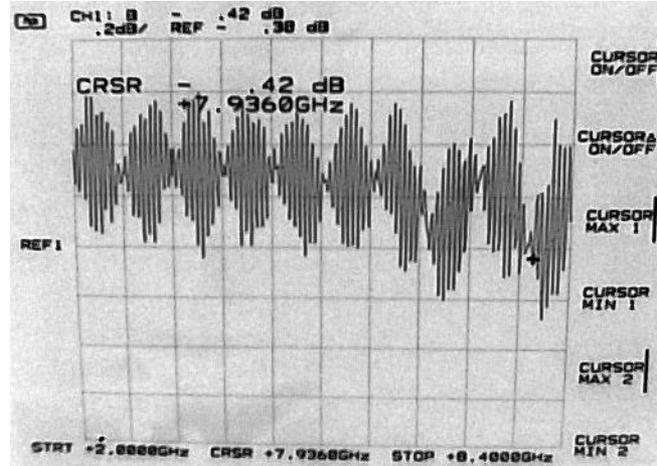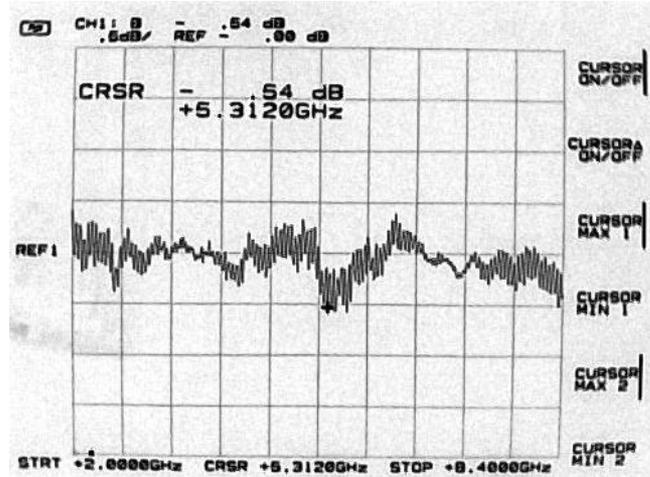

#4

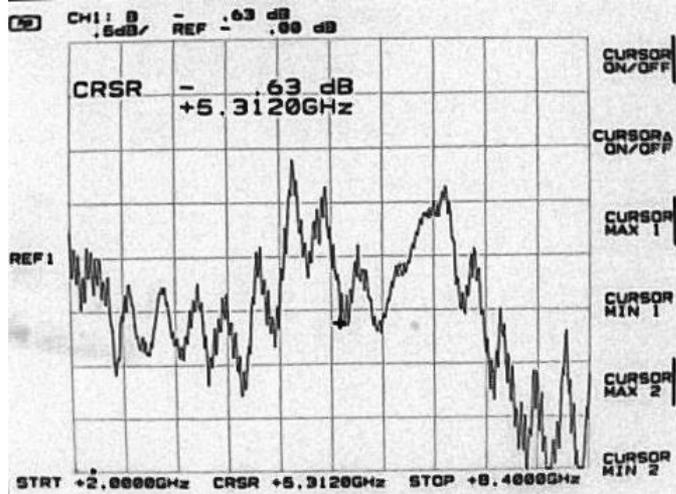


#6

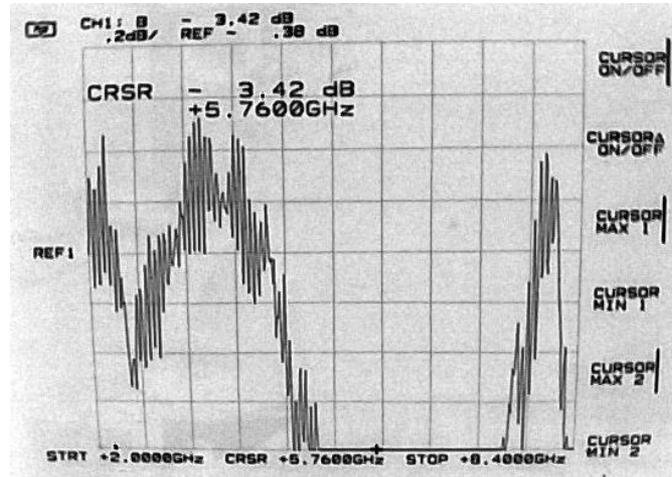

CONCLUSION


- This has been a collection of my experiences.
- I hope it has been of some benefit to you.
- Questions?

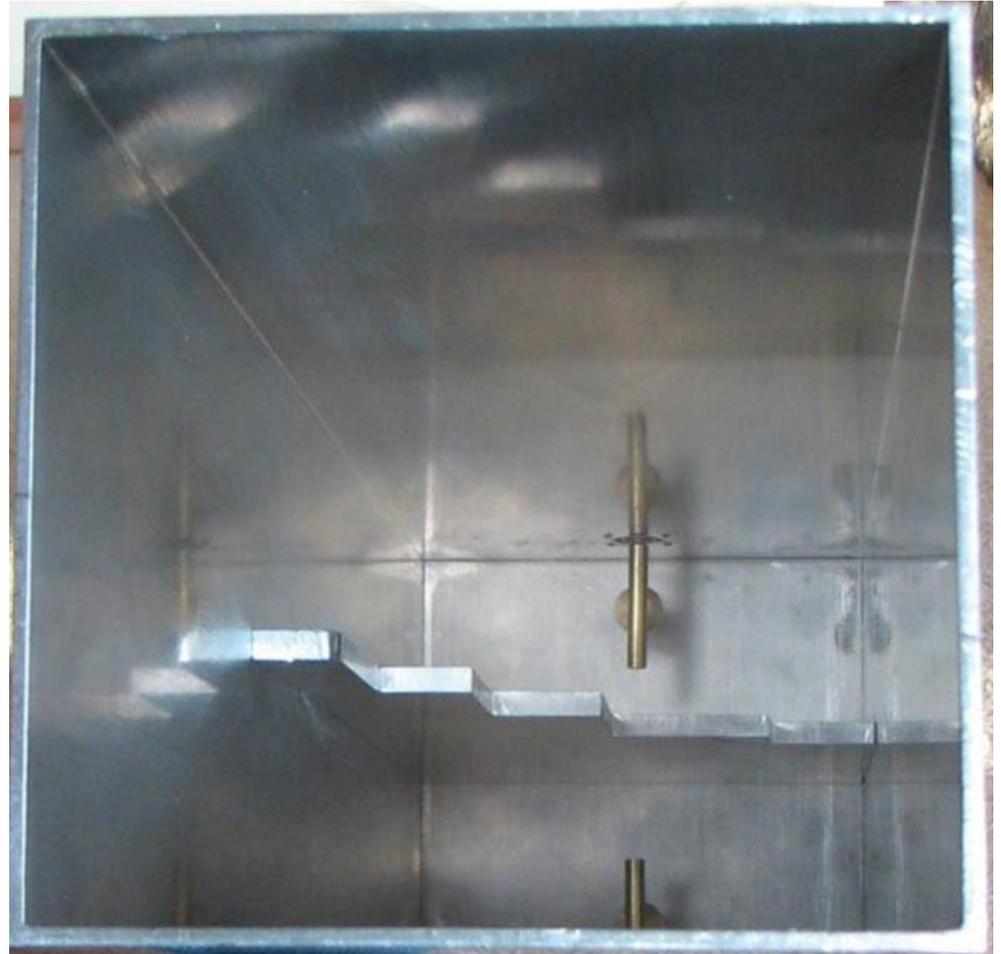A NEW TECHNIQUE FOR CONSTRUCTION OF 23CM SEPTUM FEED



COMPONENTS

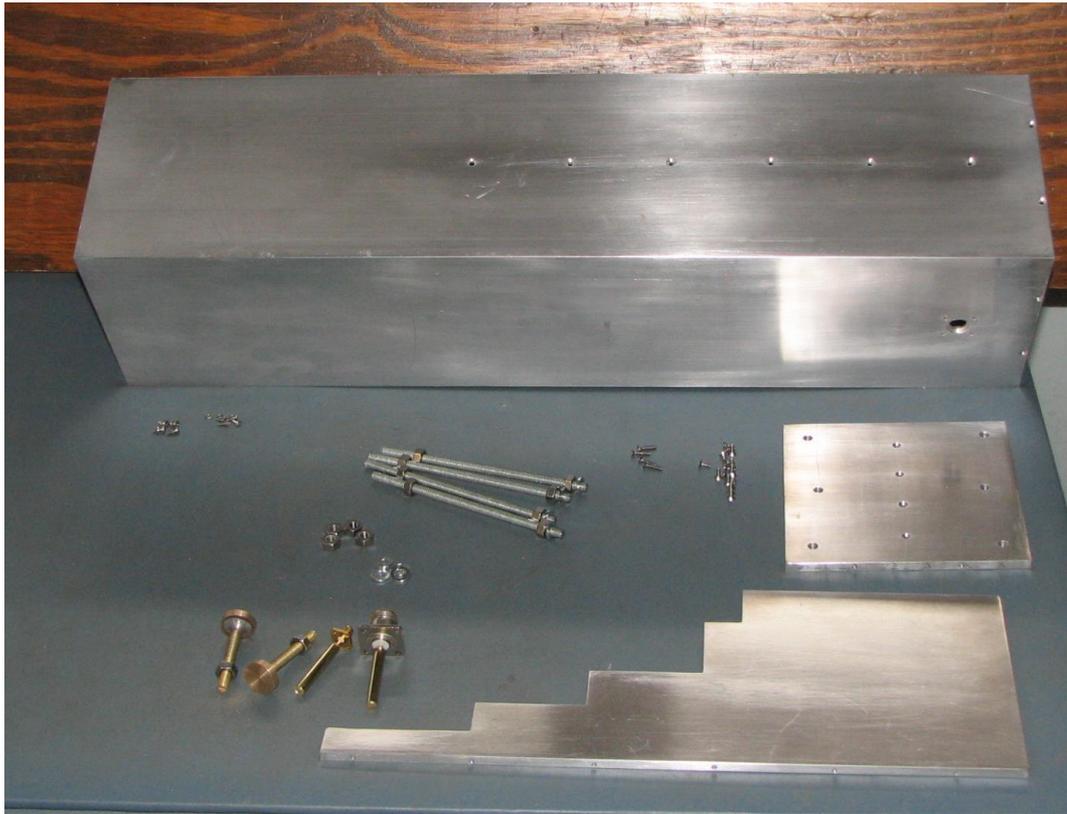Key component is 6" square tubing from On-Line Metals
(see link at <http://ptt-ak.com>)



MOUNTING



CLOSE UP



COMPARISON

- Easier to construct than sheet metal square septum feed or VE4MA feed
- Easy to tune by adjusting both probes for best VSWR
- Good circularity with no adjustments (versus labor intensive polarizer screws)
- When scalar ring is added, and the feed is compared with a VE4MA feed on a 22 ft. dish, only 0.3dB less sun noise (W5LUA & K5GW, August 2005).
- Material cost less than \$75 (Less than \$100 with shipping)

CONCLUSIONS

- See for yourself
- I brought one with me
- Detailed construction instructions in the proceedings